


Name _____
 Regents Physics

Unit 11: Electricity
 Mr. Mellon

PARALLEL CIRCUIT PRACTICE

Remember that in a parallel circuit:

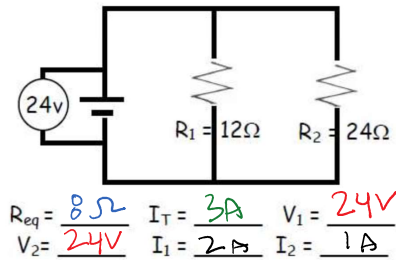- the **current** in the branches of the circuit (is the same or adds up).
- the **voltage** drops across each branch (is the same or adds up to) the total voltage.
- to calculate total **resistance**, (add or use reciprocals).




	V	I	R	P
1	24V	2A	12Ω	
2	24V	1A	24Ω	
T	24V	3A	8Ω	

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{12\Omega} + \frac{1}{24\Omega} \right)^{-1} = 8\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{24V}{8\Omega} = 3A$$

$$I_1 = \frac{V_1}{R_1} = \frac{24V}{12\Omega} = 2A$$
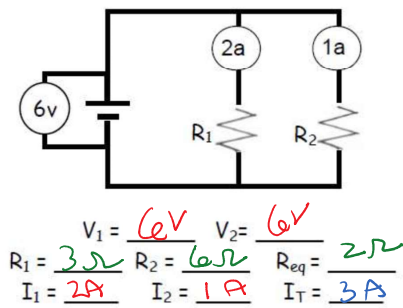
$$I_2 = \frac{V_2}{R_2} = \frac{24V}{24\Omega} = 1A$$




	V	I	R	P
1	6V	2A	3Ω	
2	6V	1A	6Ω	
T	6V	3A	2Ω	

$$I_T = I_1 + I_2 = 2A + 1A = 3A$$

$$R_1 = \frac{V_1}{I_1} = \frac{6V}{2A} = 3\Omega$$

$$R_2 = \frac{V_2}{I_2} = \frac{6V}{1A} = 6\Omega$$
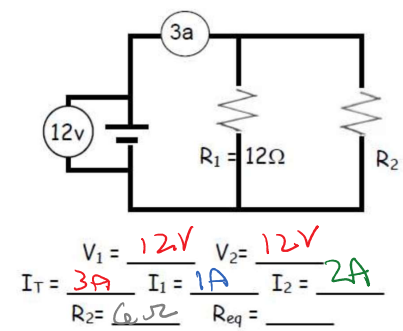
$$R_T = \frac{V_T}{I_T} = \frac{6V}{3A} = 2\Omega$$



	V	I	R	P
1	12V	1A	12Ω	
2	12V	2A	6Ω	
T	12V	3A	4Ω	

$$I_1 = \frac{V_1}{R_1} = \frac{12V}{12\Omega} = 1A$$

Unit 11 Work Packet: pg. 19


$$I_T = I_1 + I_2$$

$$I_2 = I_T - I_1$$

$$I_2 = 3A - 1A = 2A$$

$$R_2 = \frac{V_2}{I_2} = \frac{12V}{2A} = 6\Omega$$
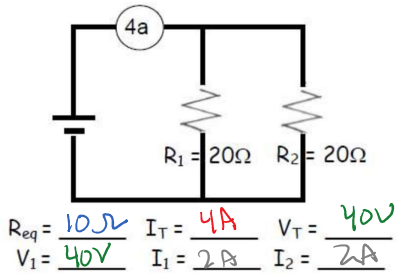
$$R_T = \frac{V_T}{I_T} = \frac{12V}{3A} = 4\Omega$$



	V	I	R	P
1	40V	2A	20Ω	
2	40V	2A	20Ω	
T	40V	4A	10Ω	


$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{1}{20\Omega} + \frac{1}{20\Omega} \right)^{-1} = 10\Omega$$

$$V_T = I_T R_T = (4A)(10\Omega)$$

$$V_T = 40V$$

$$I_1 = \frac{V_1}{R_1} = \frac{40V}{20\Omega} = 2A$$
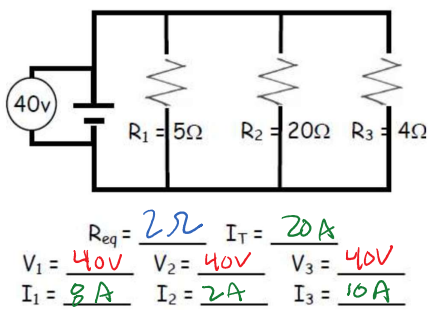
$$I_2 = \frac{V_2}{R_2} = \frac{40V}{20\Omega} = 2A$$




	V	I	R	P
1	40V	8A	5Ω	
2	40V	2A	20Ω	
3	40V	10A	4Ω	
T	40V	20A	2Ω	

$$R_T = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

$$R_T = \left(\frac{1}{5\Omega} + \frac{1}{20\Omega} + \frac{1}{4\Omega} \right)^{-1} = 2\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{40V}{2\Omega} = 20A$$
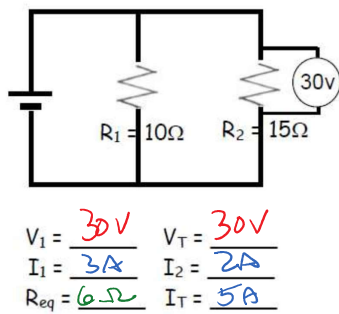
$$I_1 = \frac{V_1}{R_1} = \frac{40V}{5\Omega} = 8A$$



	V	I	R	P
1	30V	3A	10Ω	
2	30V	2A	15Ω	
T	30V	5A	6Ω	

$$I_1 = \frac{V_1}{R_1} = \frac{30V}{10\Omega} = 3A$$

$$I_2 = \frac{V_2}{R_2} = \frac{30V}{15\Omega} = 2A$$

$$I_T = I_1 + I_2 = 3A + 2A = 5A$$

$$R_T = \frac{V_T}{I_T} = \frac{30V}{5A}$$

$$R_T = 6\Omega$$