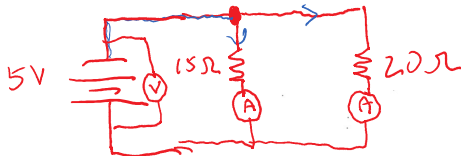


Name _____
Parallel Circuit

Regents Physics
Electricity Unit

1. A 15 ohm and a 20 ohm resistor are connected in parallel to a battery that provides a potential difference of 5 V.
A) Draw a circuit diagram. Include ammeters to measure the current through each resistor and a voltmeter to measure the total potential difference.



$$R = \frac{V}{I}$$

	V	I	R	P
1	5V	0.333A	15Ω	
2	5V	0.25A	20Ω	
T	5V	0.583A	8.57Ω	

- B) The current, potential difference, or resistance is the same through each resistor. (circle one)

- C) Calculate the equivalent resistance.

$$\left(\frac{1}{R_{eq}}\right)^{-1} = \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1} \rightarrow R_{eq} = \left(\frac{1}{15\Omega} + \frac{1}{20\Omega}\right)^{-1}$$

$$R_{eq} = \left(\frac{1}{15\Omega} + \frac{1}{20\Omega}\right)^{-1} = 8.57\Omega$$

- D) Calculate the total current in the circuit.

$$R = \frac{V}{I} \rightarrow I_T = \frac{V_T}{R_T} = \frac{5V}{8.57\Omega} = 0.583A$$

- E) Calculate the current through each resistor.

$$I_1 = \frac{V_1}{R_1} = \frac{5V}{15\Omega} = 0.333A \quad I_2 = \frac{V_2}{R_2} = \frac{5V}{20\Omega} = 0.25A$$

- F) What does the sum of these currents add up to? (Does this make sense)

$$I_1 + I_2 = 0.333A + 0.25A = 0.583A$$

→ yes, adds up to total

- G) Calculate the total amount of power used by the circuit

$$P = I_T V_T = (0.583A)(5V) = 2.92W$$

- H) Calculate the amount of energy used by circuit if it was one for 120 s.

$$W = Pt = (2.92W)(120s) = 350J$$

2. A parallel circuit is made of two resistors and has a total resistance of 5 ohms. If the resistance for one resistor is 20 ohms, calculate the resistance for the second.

$$R_1 = 20\Omega$$

$$R_T = 5\Omega$$

$$R_2 = ?$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \left(\frac{1}{R_2}\right)^{-1} = \left(\frac{1}{R_{eq}} - \frac{1}{R_1}\right)^{-1}$$

$$R_2 = \left(\frac{1}{R_{eq}} - \frac{1}{R_1}\right)^{-1}$$

$$R_2 = \left(\frac{1}{5\Omega} - \frac{1}{20\Omega}\right)^{-1}$$

$$R_2 = 6.67\Omega$$

Unit 11 Work Packet: pg.18